


1. Half Adder

- The half adder adds digits A and B.
- It has two outputs S
- The carry signal rep. into the next digit of addition.

Truth Table :

Inputs		Outputs	
A	B	Sum	Carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

Using basic gate


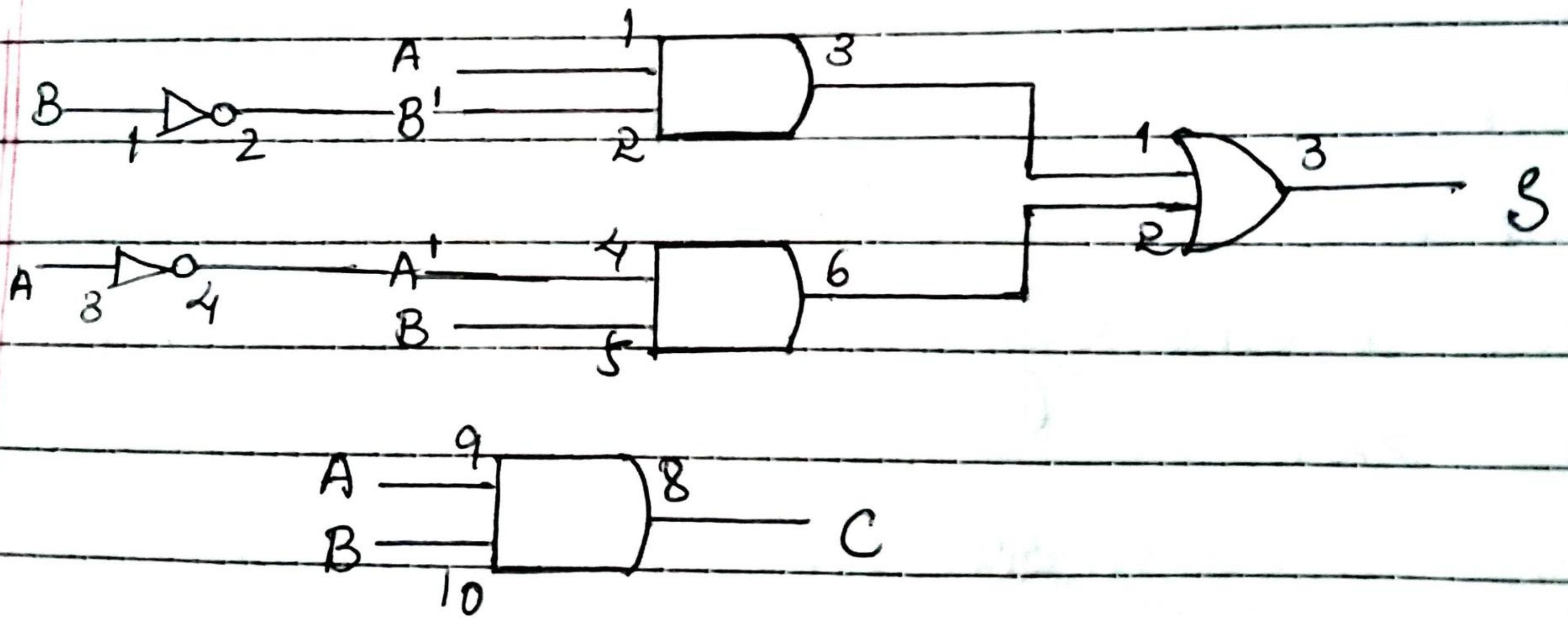


• Full Adder [Using K-map].

Input			Output	
A	B	C _{IN}	C _{OUT}	Sum
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1


2. Full Adder

Sum :

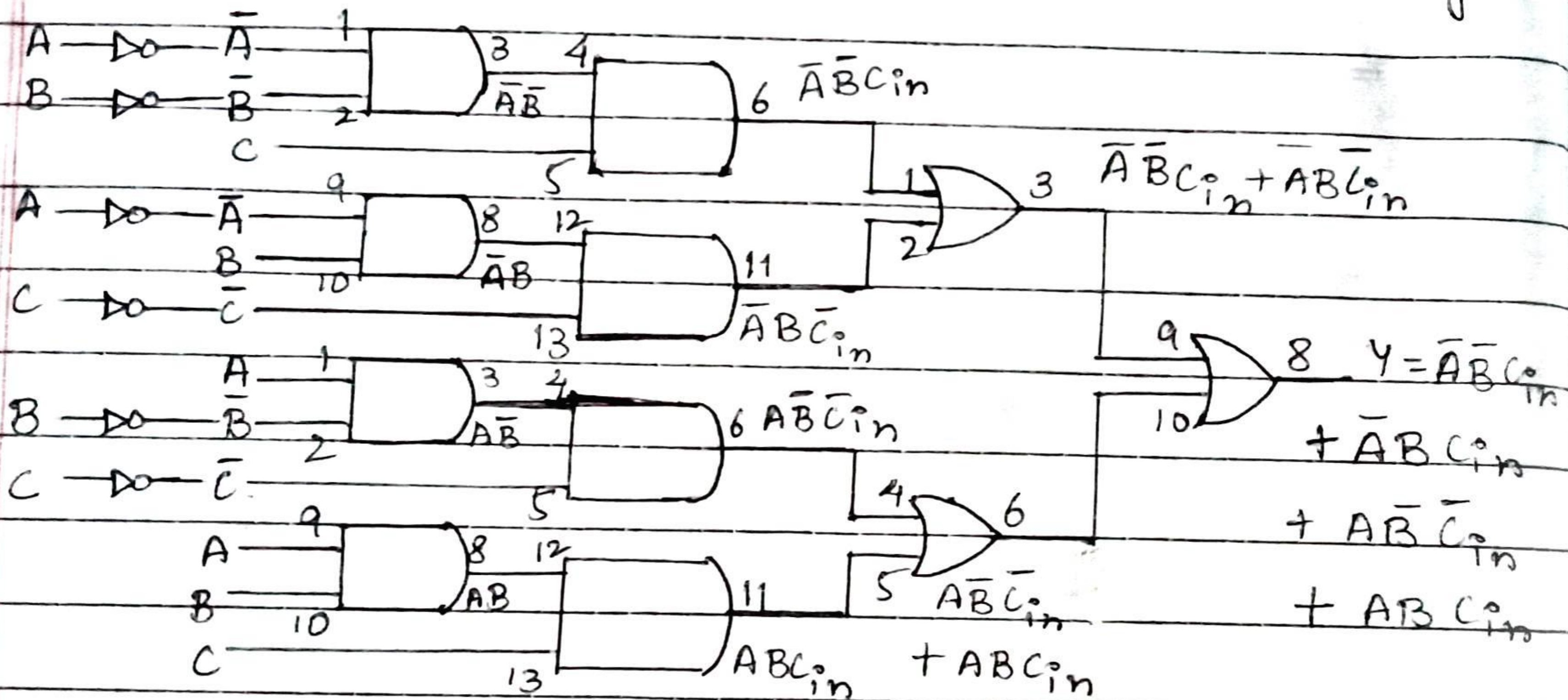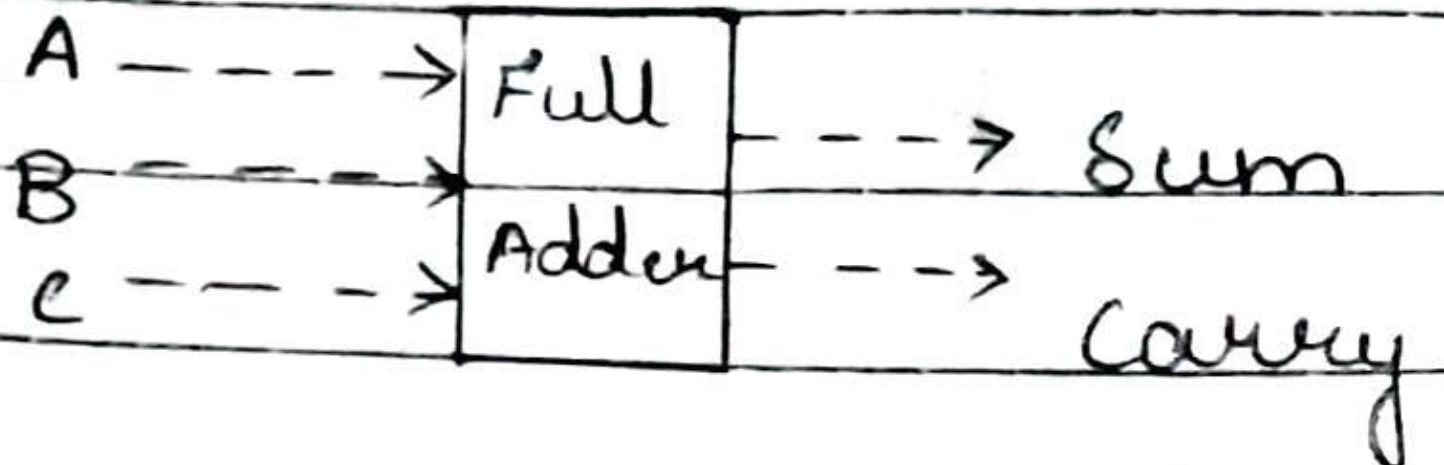

Carry :

$$Y = A \oplus B \oplus C_{in}$$

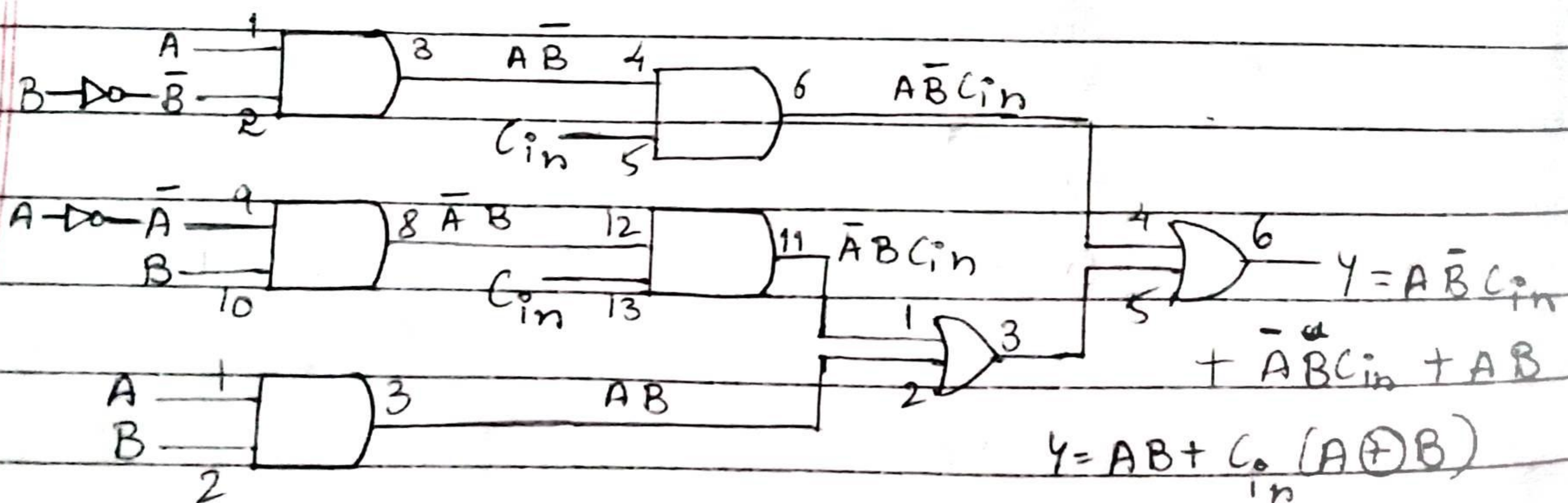


3. Half Subtractor

- Half subtractor subtracts two single digits A & B.
- It has two outputs difference (D) and borrow (B).
- Borrow signal represents the borrow for the next digit of multi digit subtraction.

Truth Table:

Inputs		Outputs	
A	B	Diff	Borrow
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0


Using AND-OR :

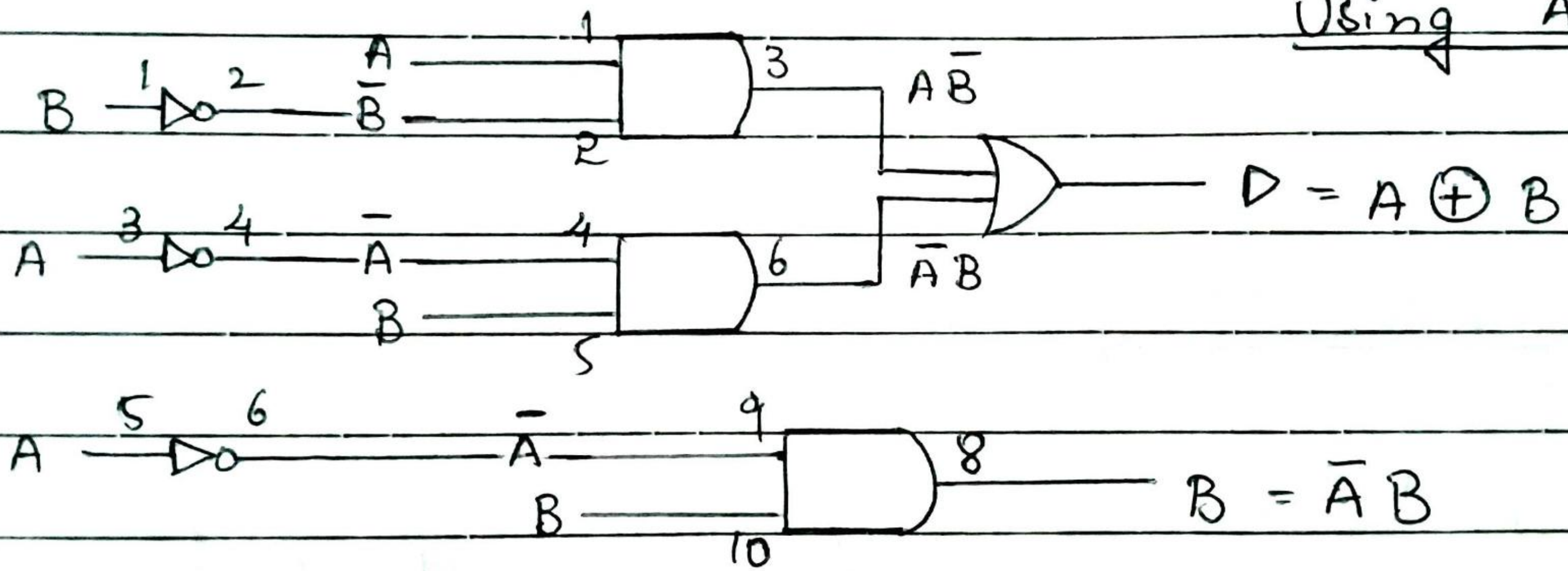


4. Full Subtractor

Truth Table :

Input			Output	
A	B	C_{in}	Bor	D
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	1	0
1	0	0	0	1
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

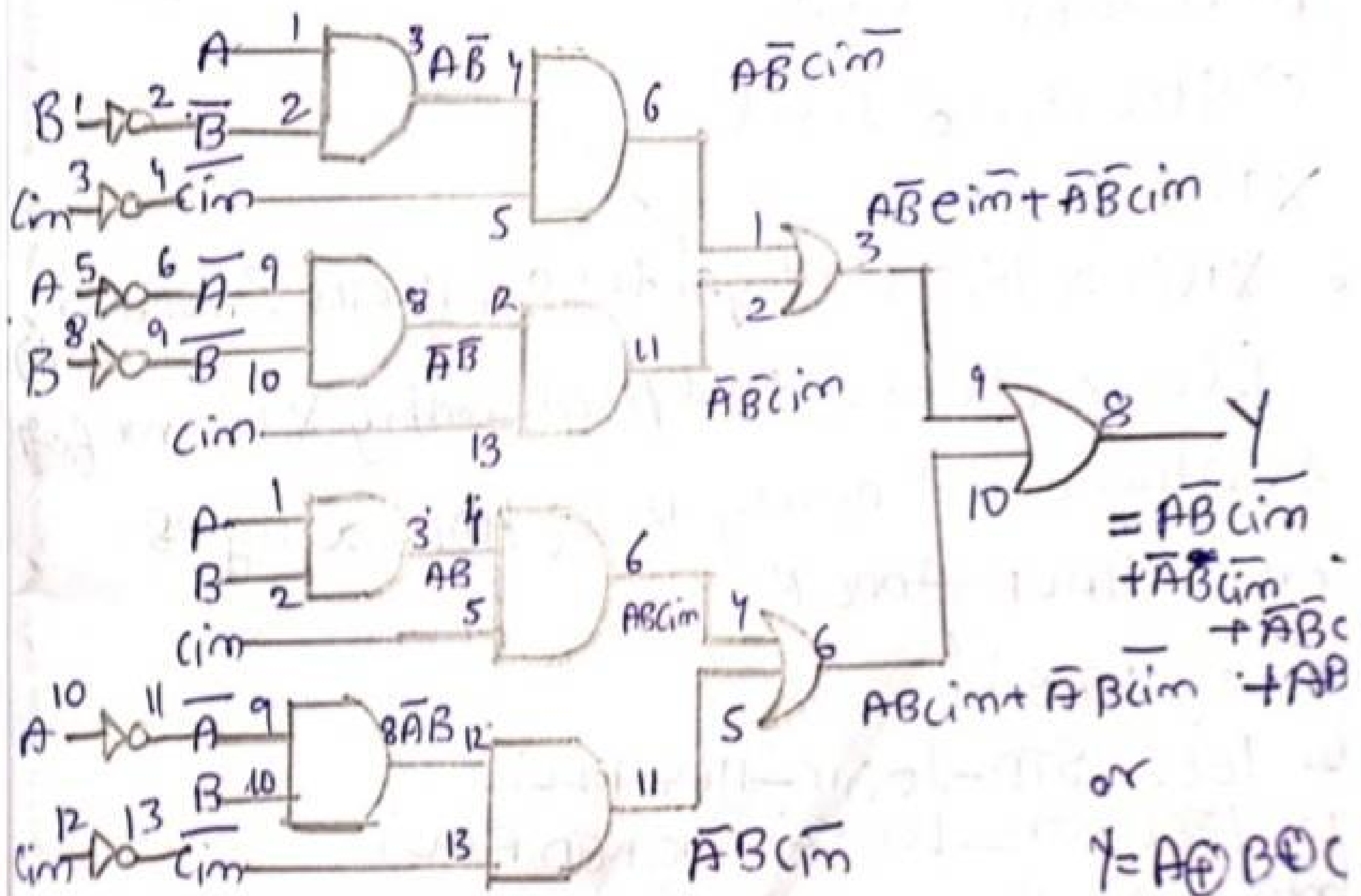

Scanned with CamScanner

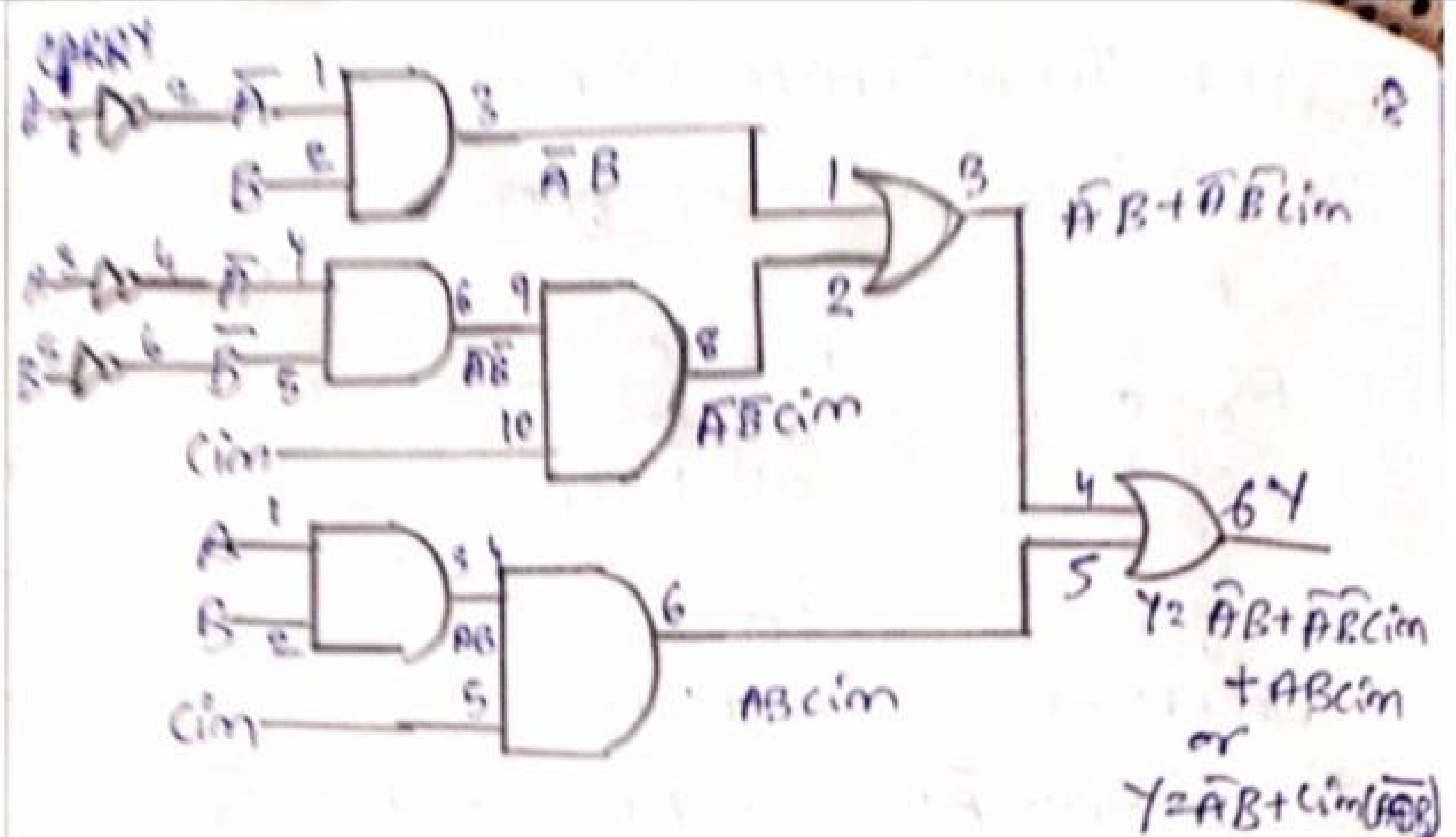


Scanned by TapScanner

Binary Input				Gray Code Output			
B ₃	B ₂	B ₁	B ₀	G ₃	G ₂	G ₁	G ₀
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1
0	0	1	0	0	0	1	1
0	0	1	1	0	0	1	0
0	1	0	0	0	1	1	0
0	1	0	1	0	1	1	1
0	1	1	0	0	1	0	1
0	1	1	1	0	1	0	0
1	0	0	0	1	1	0	0
1	0	0	1	1	1	0	1
1	0	1	0	1	1	1	1
1	0	1	1	1	1	1	0
1	1	0	0	1	0	1	0




1	1	0	1	1	0	1	1	
1	1	1	0	1	0	0	1	
1	1	1	0	1	0	0	0	

K-man⁶

B3 B2 B1 B0

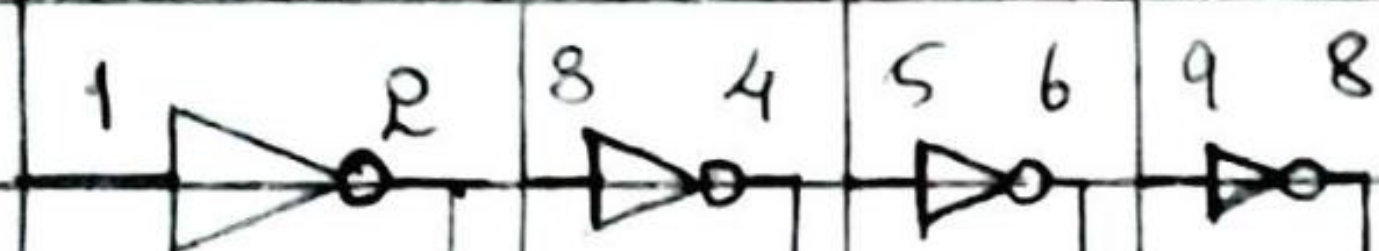

C3

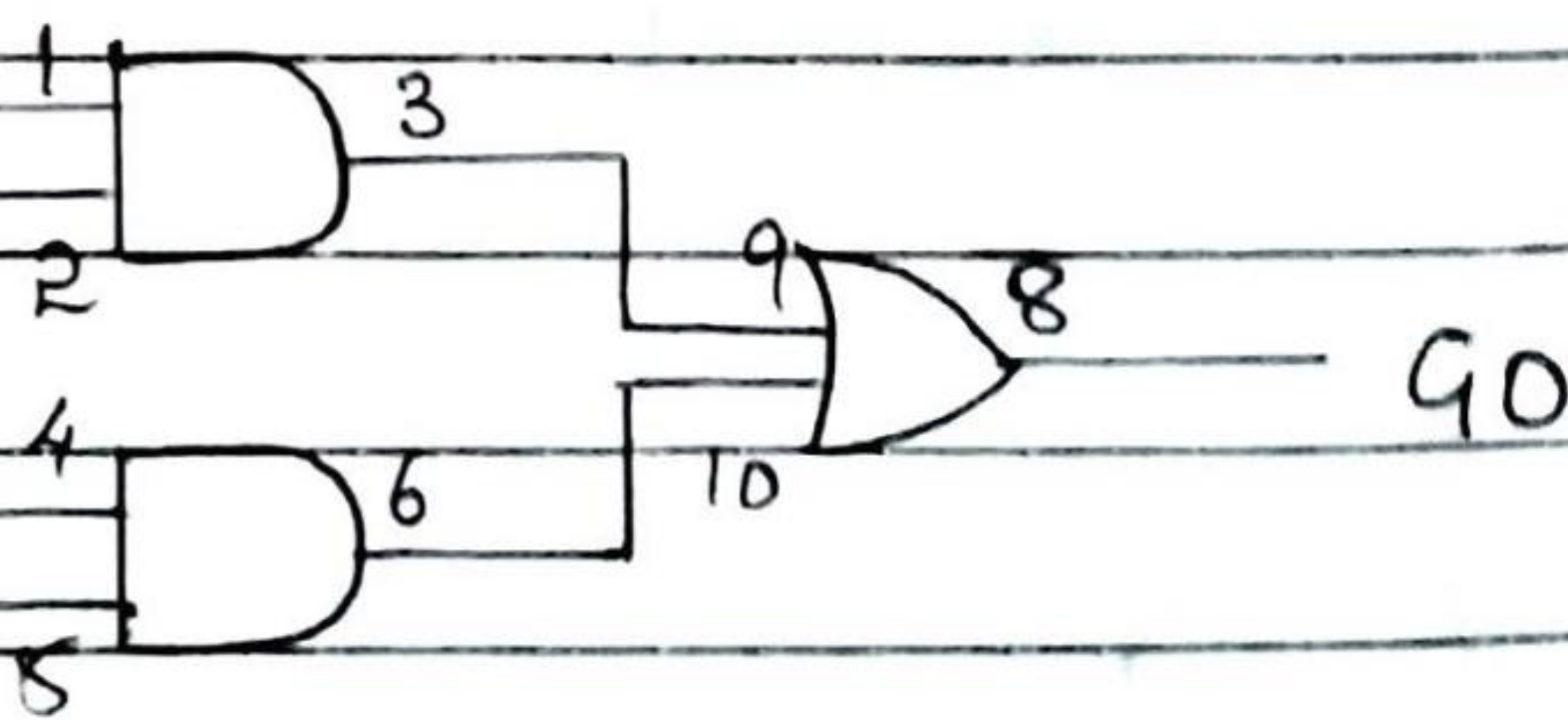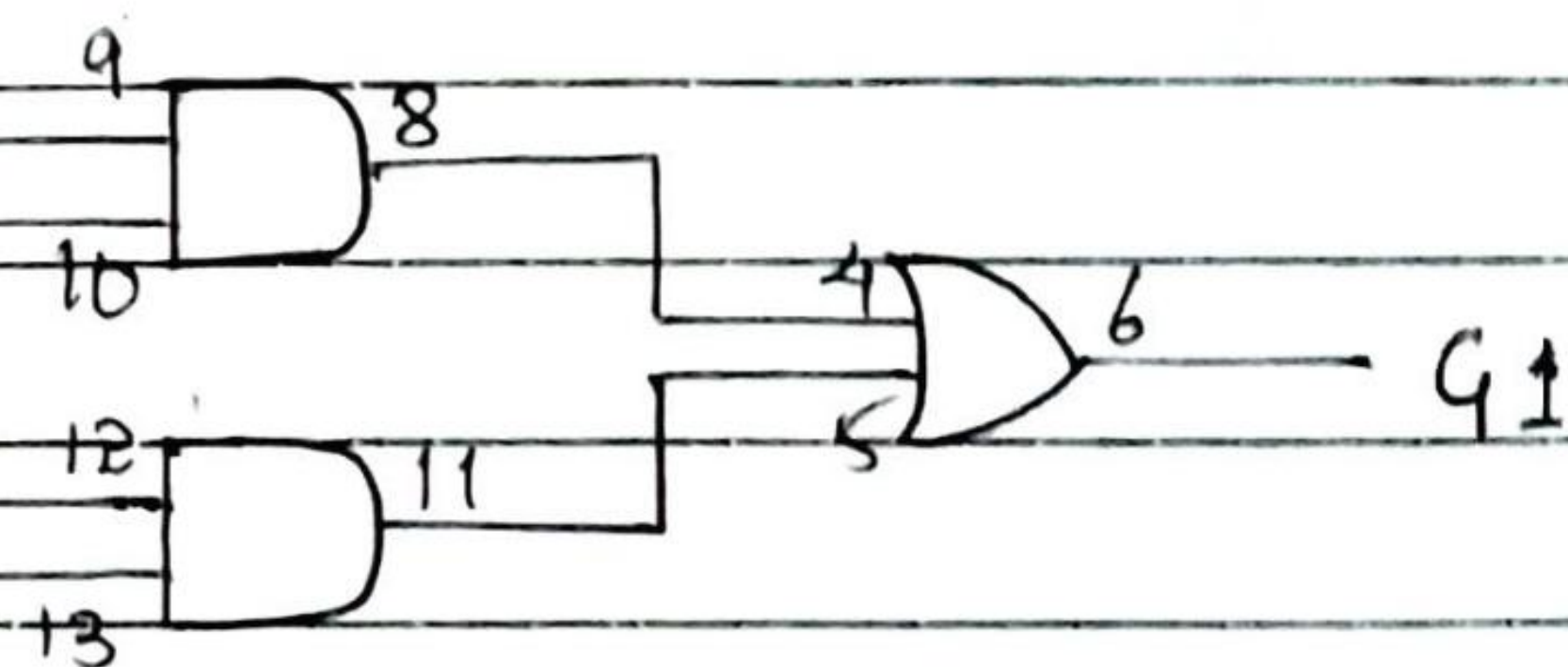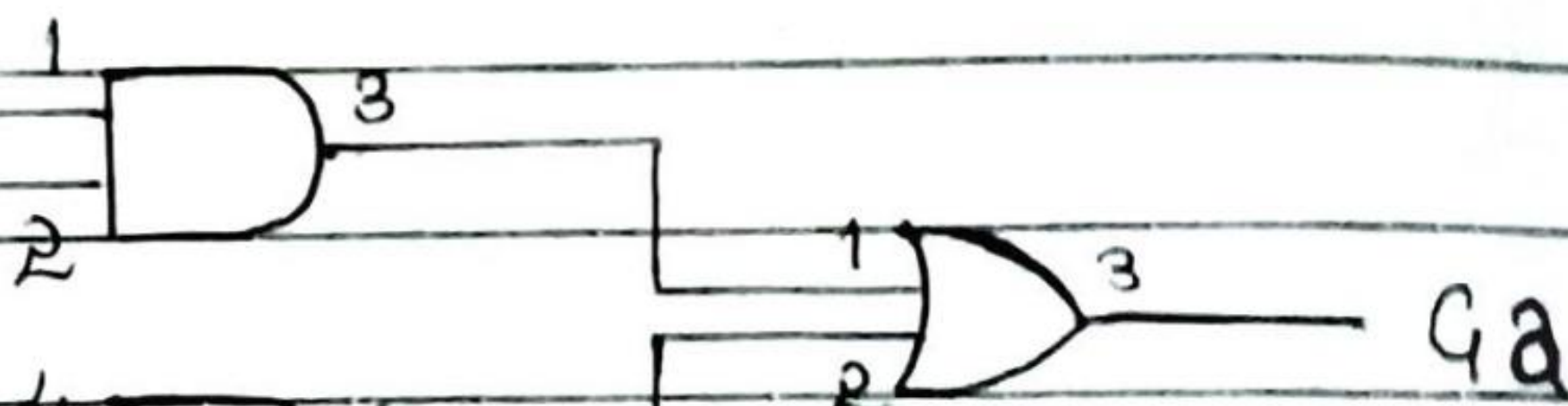

Gray to Binary:

Gray Code Input				Binary Code Output			
G ₃	G ₂	G ₁	G ₀	B ₃	B ₂	B ₁	B ₀
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1
0	0	1	1	0	0	1	0
0	0	1	0	0	0	1	1
0	1	1	0	0	1	0	0

0	1	1	1	0	1	0	1
0	1	0	1	0	1	1	0
0	1	0	0	0	1	1	1
1	1	0	0	1	0	0	0
1	1	0	1	1	0	0	1
1	1	1	1	1	0	0 1	0
1	1	1	0	1	0	1	1
1	0	1	0	1	1	0	0
1	0	0 1	1	1	1	0	1
1	0	0	0 1	1	1	1	0
1	0	0	0	1	1	1	1

$G_3 \quad G_2 \quad G_1 \quad G_0$ 