 


CAB 4: Given any 4 variable logic expression,
Simplify using Entered Variable Map and realize
the simplified logic expression using 8:1 multiplexer IC.
And implement the same in HDL.

Multiplexer

→ A multiplexer, also known as a data selector, is a device that selects between analog or digital input signals and forwards it to a single output line.

→ A multiplexer of inputs has select lines, which are used to select which input line to send to the output.



Map Entered Variable (MEV)

A Map Entered Variable is a Karnaugh Map in which the size of the map is reduced by removing one or more of the variables from the specification of map cell locations.

→ One of the input variable is placed inside Karnaugh map.

→ This reduces the Karnaugh map size by one degree.

i.e., a 3 variables problem that requires

$2^3 = 8$ locations in Karnaugh map will require $(2)^{3-1} = 4$ locations in entered variable map.

→ This technique is particularly useful for mapping problems with more than 2 input variables.

Example:

$$f(A, B, C, D) = \sum m(2, 3, 4, 5, 13, 15) + \sum d(8, 9, 10, 11)$$

Decimal	A	B	C	D	f	MEV mapping
0	0	0	0	0	0	0 D_0
1	0	0	0	1	0	
2	0	0	1	0	1	1 D_2
3	0	0	1	1	1	
4	0	1	0	0	1	1 D_3
5	0	1	0	1	1	
6	0	1	1	0	0	0 D_3
7	0	1	1	1	0	
8	1	0	0	0	X	X D_4
9	1	0	0	1	X	
10	1	0	1	0	X	X D_5
11	1	0	1	1	X	
12	1	1	0	0	0	0 D_6
13	1	1	0	1	1	
14	1	1	1	0	0	0 D_7
15	1	1	1	1	1	


8:1 multiplexer IC
Pin details - IC 74151.

74 x x 151

7	\overline{EN}	
11	C (LSB)	
10	B	
9	A (MSB)	
4	D_0	
3	D_1	5 γ
2	D_2	6 $\overline{\gamma}$
1	D_3	
15	D_4	
14	D_5	
13	D_6	
12	D_7	

8:1 Multiplexer


Circuit Diagram:

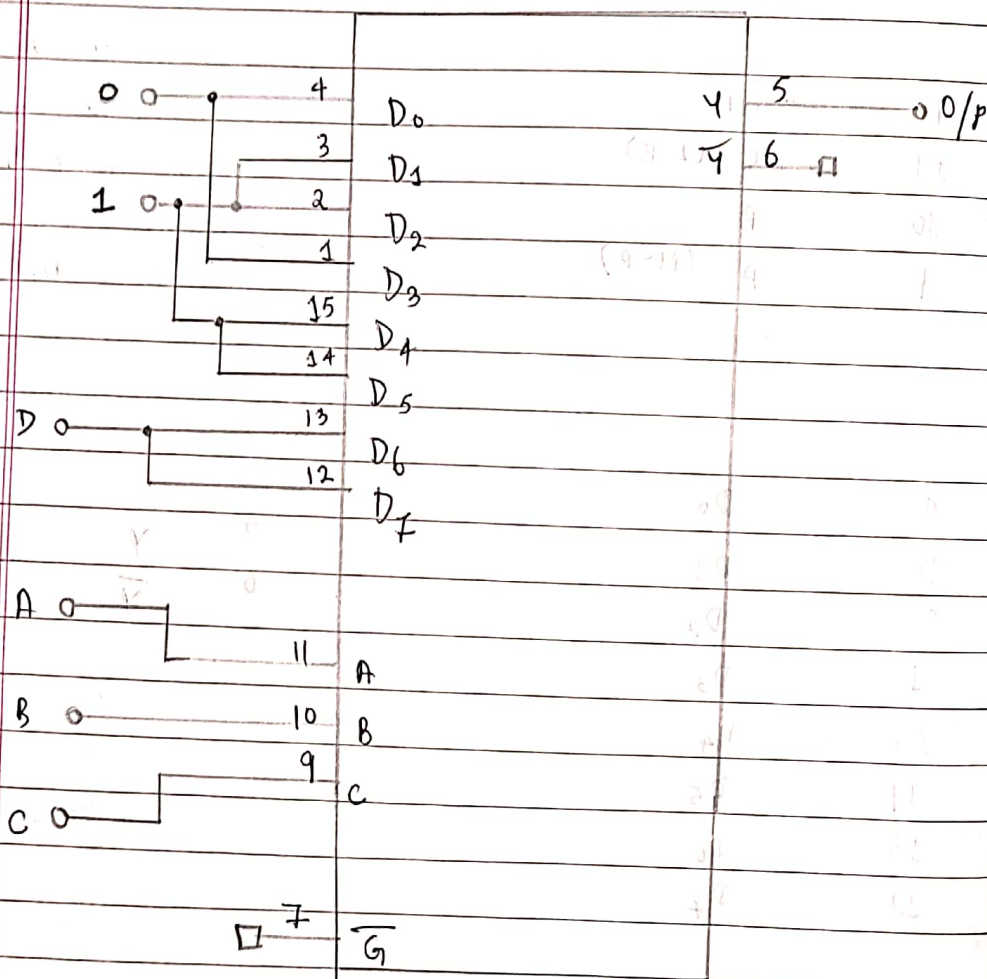

Multiplexer.

classmate

Date _____
Page _____

 

```
library IEEE;  
use IEEE.STD_LOGIC_1164.ALL;  
use IEEE.STD_LOGIC_ARITH.ALL;  
use IEEE.STD_LOGIC_UNSIGNED.ALL;
```

```
entity mmm is
```

```
Port (i: in std_logic_vector (7 downto 0);  
      sel: in std_logic_vector (2 downto 0);  
      z: out std_logic);
```


```
end mmm;
```

```
architecture Behavioral of mmm is
```

```
begin
```

```
z <= i(0) when sel = "000" else  
i(1) when sel = "001" else  
i(2) when sel = "010" else  
i(3) when sel = "011" else  
i(4) when sel = "100" else  
i(5) when sel = "101" else  
i(6) when sel = "110" else  
i(7)
```

```
end Behavioral;
```

 Code.

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;
```

entity adder is

```
Port ( A : in std_logic;
       B : in std_logic;
       SUM : out std_logic;
       CARRY : out std_logic );
```

end adder;

architecture Behavioral of adder is

begin

SUM <= A XOR B;

CARRY <= A AND B;


end Behavioral.

Full Adder

classmate

Date

Page

 

Code:

library IEEE;

use IEEE STD LOGIC 1164 ALL;

use IEEE STD LOGIC ARITH ALL;

use IEEE STD LOGIC UNSIGNED ALL;

entity FADD is

port (A: in std_logic;

B: in std_logic;

C: in std_logic;

SUM: out std_logic;

CARRY: out std_logic);

end FADD;

architecture Behavioural of FADD is

begin

SUM <= A XOR B XOR C;

CARRY <= (A AND B) OR (C AND (A XOR B))

end Behavioural;