
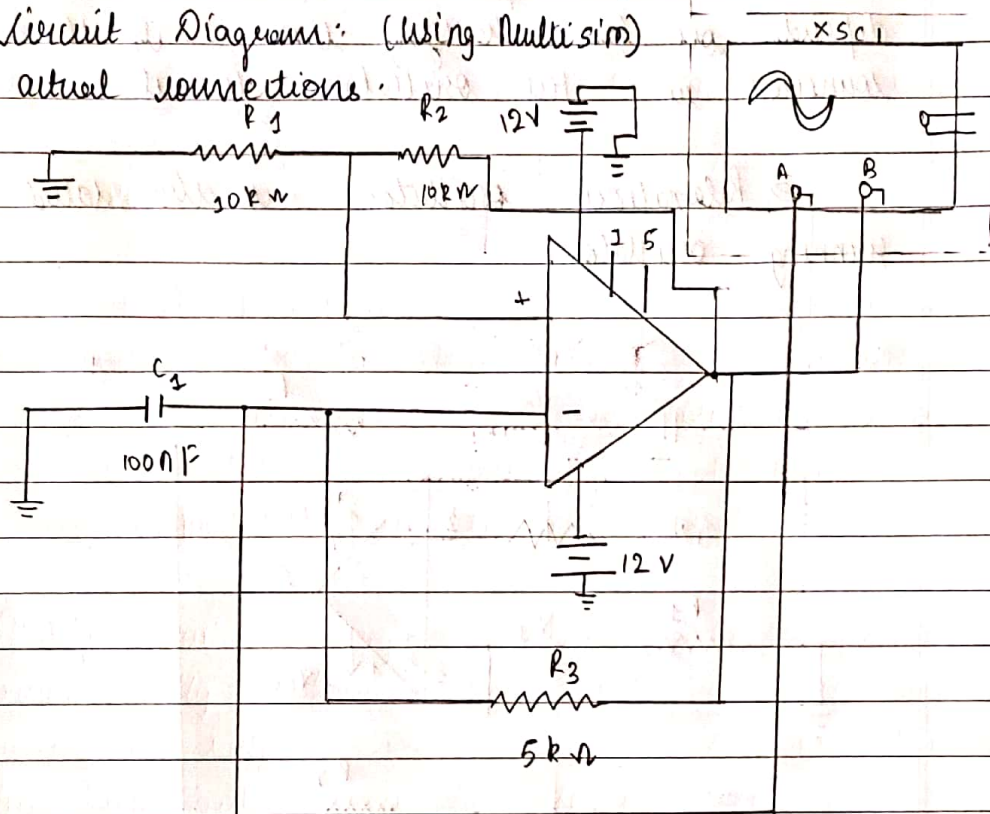


To design and implement a rectangular waveform generator (op-amp relaxation oscillator) for a given frequency.

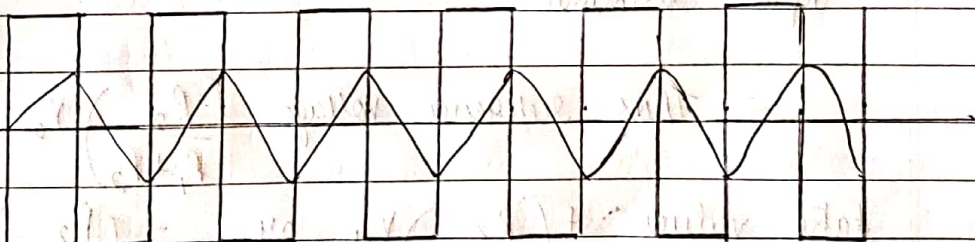Circuit Diagram: (Using Multisim)
And actual connections.




Waveform:



Relaxation oscillator: Is a non-linear electronic oscillator circuit that generates a continuous non-sinusoidal output signal in the form of rectangular wave, triangular wave or a saw-tooth wave. The time period of non-sinusoidal output depends on the charging time of the capacitor connected in the oscillator circuit.

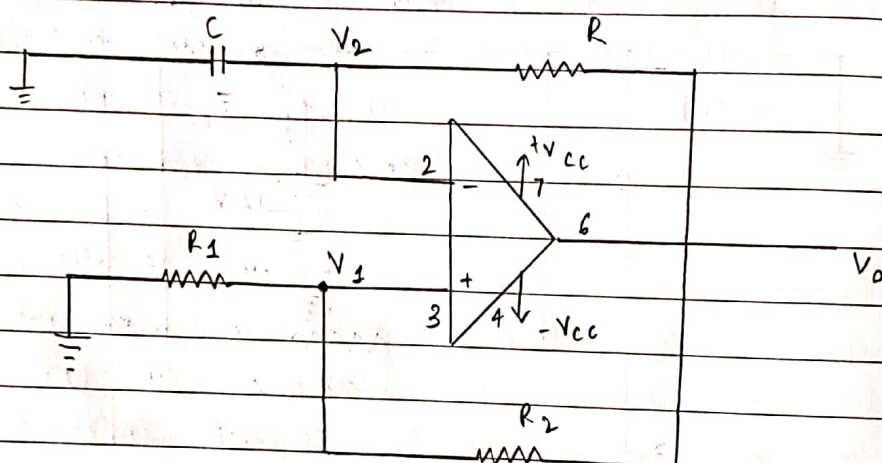→ Relaxation oscillator is also called as free running oscillator.



→ In this figure the op-amp operates in the saturation region. Here, a fraction $\left(\frac{R_2}{R_1 + R_2}\right)$ of output is fed back to non inverting input terminal.

→ Thus reference voltage $\left(\frac{R_2}{R_1 + R_2}\right) V_0$ and may take values $+\left(\frac{R_2}{R_1 + R_2}\right) V_{sat}$ or $-\left(\frac{R_2}{R_1 + R_2}\right) V_{sat}$

→ The output is also fed back to the inverting input terminal after integrating by means of low-pass RC combination. Thus whenever

the voltage at inverting input terminal just exceeds reference voltage, switching takes place resulting in a square wave output.

Design:

Time period of the output waveform is given by $T = 2RC \ln \left(\frac{1+\beta}{1-\beta} \right) \rightarrow (1)$

$$\text{where } \beta = \frac{R_1}{R_1 + R_2}$$

If $R_2 = 1.16 R_1$, then $\beta = 0.463$

$$\text{From (1), } T = 2RC \ln \left(\frac{1.463}{0.537} \right) = 2RC \ln(e)$$

$$T = 2RC$$

$$R = \frac{T}{2C} \rightarrow (2)$$

For given frequency of 1 kHz.

$$T = \frac{1}{f} = \frac{1}{1000} = 1 \times 10^{-3} \text{ s}$$

If we take $R_1 = 10 \text{ k}\Omega$ and $R_2 = 11.6 \text{ k}\Omega$

If we take $C = 0.1 \mu\text{F}$

then from (2)


$$R = \frac{T}{2C} = \frac{10^{-3}}{2 \times 0.1 \times 10^{-6}} = 5 \text{ k}\Omega$$

The voltage across the capacitor has a peak voltage of $V_c = \frac{R_1}{R_1 + R_2} V_{sat}$

$$V_{sat} = 90\% V_{cc} \\ = \frac{90}{100} \times 15 = 13.5 \approx 12V$$


$$V_c = \frac{10}{10 + 11.6} \times 12 = 5V$$

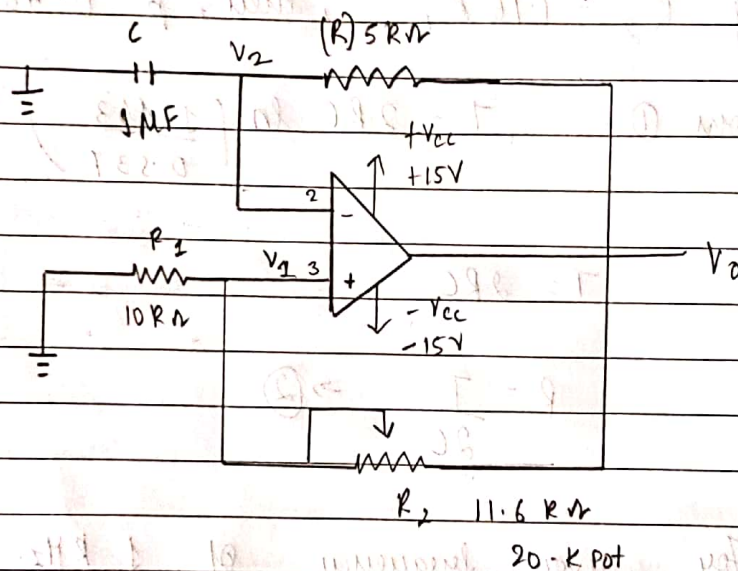Relaxation oscillator : circuit diagram and actual connection



Waveforms .

O/P
waveform

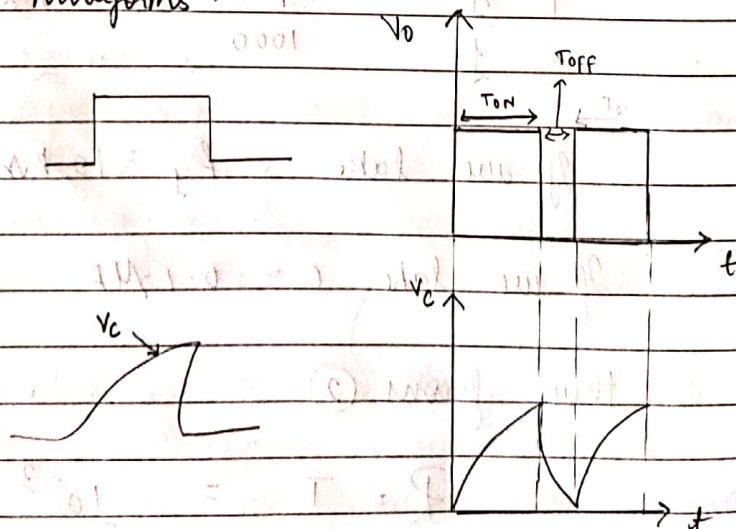

Capacitor
waveform

Relaxation Oscillator

Result :

Sl No	f KHz	R	
1	1 KHz	5 k Ω	5 V
2	1.5 KHz	3.335 k Ω	5 V
3	2 KHz	2.5 k Ω	5 V

$$\underline{R} = \frac{I}{2C} = \frac{0.667 \times 10^{-3}}{2 \times 0.1 \times 10^{-6}} \quad T = \frac{1}{1.5 \times 10^3}$$

$$= 3.335 \text{ k}\Omega$$

$$\underline{R} = \frac{I}{2C} = \frac{0.5 \times 10^{-3}}{2 \times 0.1 \times 10^{-6}} \quad T = \frac{1}{2 \times 10^3}$$

$$= 2.5 \times 10^3 \Omega$$